


First Order System Rise Time by Robert L Rauck

Analog designers are often called upon to design an amplifier to meet a specific rise time requirement. Amplifiers with feedback loops that exhibit a first order roll-off are the easiest to characterize. One of the rules of thumb often used in such cases is the following equation:

$$t_r = \frac{0.35}{BW}$$

where BW is the bandwidth of an amplifier employing feedback with a first order loop gain roll-off.

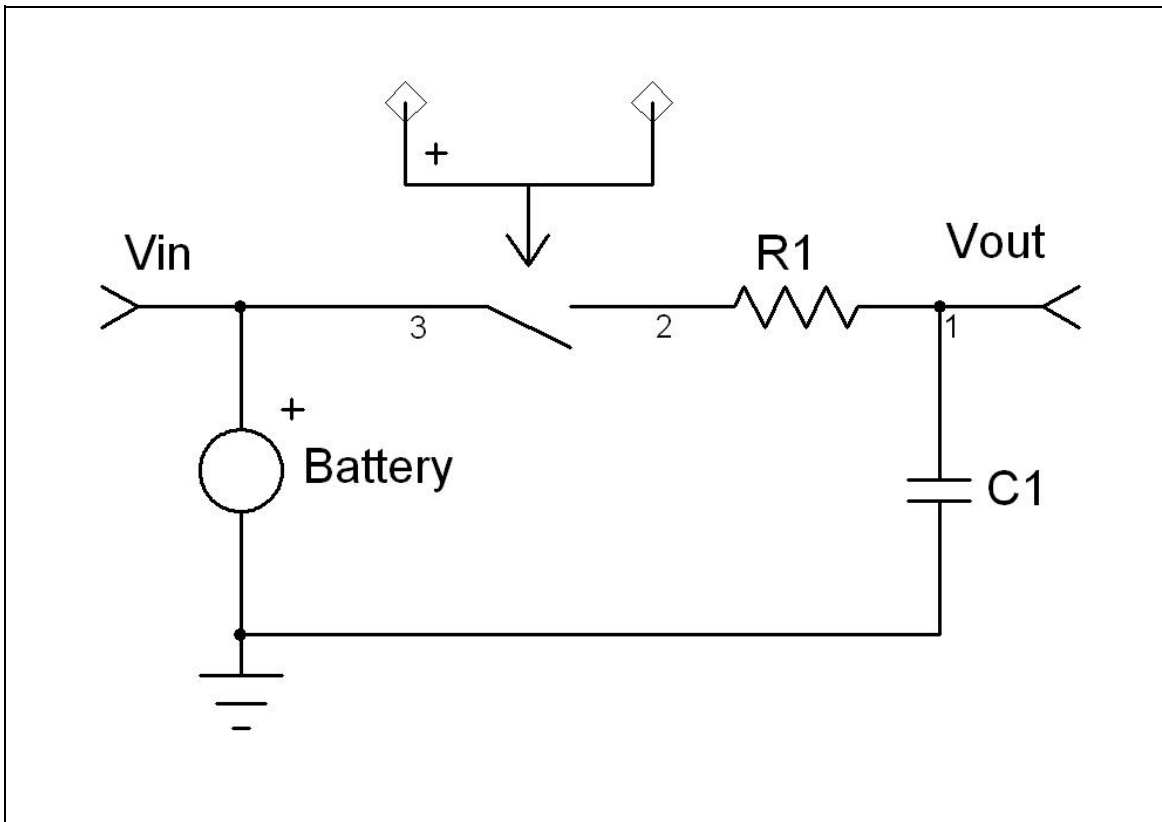This expression is used all the time but many engineers do not know where it came from or how to derive it. The origin of this expression arises from the behavior of a R-C network when excited by a step input.



Let's write an expression for the behavior of this circuit at switch closure using Laplace Transform notation. The circuit input is a step function due to the presence of the switch. We will assume the capacitor is initially uncharged.

$$\frac{V_{in_t0_plus}}{s} = I(s) \cdot R + \frac{I(s)}{s \cdot C}$$

$$\frac{V_{in_t0_plus}}{s} = \left(\frac{s \cdot R \cdot C + 1}{s \cdot C} \right) \cdot I(s) = (s \cdot R \cdot C + 1) \cdot V_C(s)$$

$$V_C(s) = V_{in_t0_plus} \cdot \frac{\frac{1}{R \cdot C}}{s \cdot \left(s + \frac{1}{R \cdot C} \right)} = V_{in_t0_plus} \cdot \left[\frac{\omega}{s \cdot (s + \omega)} \right]$$

Now let's take the inverse transform.

$$V_C(t) = V_{in_t0_plus} \cdot \left(1 - e^{-\frac{t}{R \cdot C}} \right)$$

From here forward we will refer to the input voltage as V_{in} since it is a constant. In this circuit, the capacitor voltage is the output voltage. Therefore:

$$V_{out}(t) = V_{in} \cdot \left(1 - e^{-\frac{t}{\tau}} \right)$$

$$R := 1000$$

$$C := 15.9 \cdot 10^{-6}$$

$$\tau := R \cdot C$$

Here a specific corner frequency has been picked to stimulate the discussion.

$$\frac{V_{out}(t)}{V_{in}} = 1 - e^{-\frac{t}{\tau}}$$

$$f_c := \frac{1}{2 \cdot \pi \cdot \tau}$$

$$\tau := \frac{1}{f_c \cdot (2 \cdot \pi)}$$

$$e^{-\frac{t}{\tau}} = 1 - \frac{V_{out}(t)}{V_{in}}$$

$$\frac{-t}{\tau} = \ln \left(1 - \frac{V_{out}(t)}{V_{in}} \right)$$

$$t = -\tau \cdot \ln \left(1 - \frac{V_{out}(t)}{V_{in}} \right)$$

$$t_R = -\tau \cdot \ln(1 - 0.9) + \tau \cdot \ln(1 - 0.1)$$

$$t_R = \tau \cdot (\ln(0.9) - \ln(0.1))$$

$$\ln(0.9) - \ln(0.1) = 2.197225$$

The rise time of an R-C circuit is approximately $2.2 \cdot \tau$ as we all know from experience.

$$t_R := (\ln(0.9) - \ln(0.1)) \cdot \tau$$

$$t_R := \frac{(\ln(0.9) - \ln(0.1))}{f_c}$$

$$\frac{(\ln(0.9) - \ln(0.1))}{(2 \cdot \pi)} = 0.349699$$

Clearly the rise time of an R-C circuit can be expressed as approximately $2.2 \times \tau$ which, as we can see, is equal to approximately 0.35 divided by the R-C corner frequency (f_c).

Now we would like to extend this discussion to include the feedback amplifier case where the R-C corner frequency is replaced in the expression by the loop cross-over frequency.

$$G_{CL} = \frac{V_{out}(t)}{V_{in}}$$

$$-\left(\frac{1-H}{H} \right) = G_{CL_Ideal}$$

This is the ideal closed Loop gain of a noninverting amplifier assuming a perfect Op Amp. This gain will be independent of frequency if the feedback network is resistive.

$$G_{CL} = -\left(\frac{1-H}{H} \right) \cdot \left(\frac{G \cdot H}{1+G \cdot H} \right)$$

This is the actual closed loop gain of the amplifier with the given Op Amp characteristics. This expression determines the gain and phase shift applied to signals processed by this amplifier. The $G \cdot H$ term does not include the DC gain inversion. That is represented by the minus sign in the equation.

Assume that G is a gain block with an embedded R-C filter to give it a first order roll-off at a frequency more than one decade below loop cross-over. Let's examine this expression at loop cross-over where $G^*H = 1$ at an angle of -90 degrees since we are more than a decade beyond the R-C corner embedded in G. The term $G^*H/(1+G^*H)$ is an error term that determines the departure of closed loop gain from the ideal gain term (flat with frequency) defined above.

$$\frac{G \cdot H}{1 + G \cdot H} = \frac{K \cdot \left(\frac{\omega}{s + \omega} \right)}{1 + K \cdot \left(\frac{\omega}{s + \omega} \right)}$$

G^*H has been replaced by a constant (K) times the Laplace Transform expression for the embedded R_C network.

Let's focus on when the magnitude of G^*H is 1 (loop cross-over frequency):

$$K \cdot \left(\frac{\omega}{s + \omega} \right) = K \cdot \left(\frac{1}{\frac{s}{\omega} + 1} \right) = \left[K \cdot \left(\frac{1}{1 + j \cdot \frac{\omega 1}{\omega}} \right) \cdot \left(\frac{1 - j \cdot \frac{\omega 1}{\omega}}{1 - j \cdot \frac{\omega 1}{\omega}} \right) \right] = \left[K \cdot \left(\frac{1}{1 + j \cdot \frac{f 1}{f}} \right) \cdot \left(\frac{1 - j \cdot \frac{f 1}{f}}{1 - j \cdot \frac{f 1}{f}} \right) \right] = K \cdot \frac{1 - j \cdot \left(\frac{f 1}{f} \right)}{1 + \left(\frac{f 1}{f} \right)^2}$$

$$\left[\frac{1 - j \cdot \left(\frac{f 1}{f} \right)}{1 + \left(\frac{f 1}{f} \right)^2} \right] = K \cdot \sqrt{\frac{1}{1 + \left(\frac{f 1}{f} \right)^2}}$$

which is ~

$$\left[\frac{1}{\left(\frac{f 1}{f} \right)} \right] = 1$$

when K is $\gg 1$ and

$$\left[\frac{f 1}{f} \right] = K$$

The loop cross-over frequency will converge to $K \cdot f$ (where f is the R-C corner freq. of the embedded R-C filter) when K is $\gg 1$. The corner frequency of the closed loop transfer function represented by this amplifier circuit will be shown to be $(K+1) \cdot f$ which is $\sim K \cdot f$ when K is $\gg 1$. Therefore we have demonstrated that the amplifier will behave like a simple R-C circuit (multiplied by a constant to account for amplifier DC gain) where the effective corner frequency is essentially the loop cross-over frequency.

$$\frac{G \cdot H}{1 + G \cdot H} = \frac{K}{K + 1} \cdot \left[\frac{\omega \cdot (K + 1)}{s + \omega \cdot (K + 1)} \right] = \frac{K}{K + 1} \cdot \left(\frac{\omega 1}{s + \omega 1} \right)$$

where $\omega 1$ is a new corner frequency is $K+1$ times that of the embedded R-C circuit. The DC value of the correction term is $K/(1+K)$ as expected. It will be noted that the frequency dependant term has the same form as that for the simple R_C network and therefore the response is identical to an equivalent R-C circuit.

The complete transfer function is therefore:

$$G_{CL} = - \left(\frac{1 - H}{H} \right) \cdot \left[\frac{K}{K + 1} \cdot \left(\frac{\omega 1}{s + \omega 1} \right) \right]$$

Now let's excite this network with the same step input as used on the simple R-C network:

$$V_{\text{out}}(s) = -\frac{V_{\text{in}_t0_plus}}{s} \cdot \left[\left(\frac{1-H}{H} \right) \cdot \left[\frac{K}{K+1} \cdot \left(\frac{\omega l}{s + \omega l} \right) \right] \right]$$

$$V_{\text{out}}(s) = -V_{\text{in}_t0_plus} \cdot \left[\left(\frac{1-H}{H} \right) \cdot \left(\frac{K}{K+1} \right) \cdot \left[\frac{\omega l}{s \cdot (s + \omega l)} \right] \right]$$

Now let's take the inverse transform:

$$V_{\text{out}}(t) = -V_{\text{in}_t0_plus} \cdot \left(\frac{1-H}{H} \right) \cdot \left(\frac{K}{K+1} \right) \cdot \left(1 - e^{-\frac{t}{\tau}} \right)$$

This expression has the same form as the transfer function of the simple R-C circuit defined above (except for the DC gain term $((1-H) / H) \cdot (K / (K+1))$). Therefore the rise time of the amplifier will have the same form as the R-C circuit. Stated another way, the loop cross-over frequency is the effective corner frequency of the amplifier closed loop transfer function. One equivalent circuit would be a frequency independent gain block in series with an equivalent R-C circuit. In this case the effective R-C corner frequency would be shifted to the loop cross-over frequency. The important thing to remember is that $G^*H / (1 + G^*H)$ of a first order roll-off loop looks like the frequency response of a simple R-C network when the ideal closed loop gain is flat with frequency.


In the schematic that follows, I have modeled an amplifier that has the characteristics we have discussed. Here B1, B2 and the R-C network are used to model an Op Amp that has an open loop gain of -10,000 and a gain roll-off at 10 Hz. B1 and B2 are user definable gain blocks that I have defined as indicated on the schematic.

If we examine the closed loop gain of this amplifier, we see that it is flat at -10 until cross-over where it begins to roll off. The DC loop gain is $G^*H = 80\text{dB} + 20 \cdot \log(R2 / (R2 + R3)) = 59.172\text{dB}$ and therefore the ratio of corner freq to cross-over freq is $10^{59.172/20} = 909.076$ times the 10 Hz corner frequency of $R1 \cdot C1$ or 9.09 kHz cross-over freq.


$$f_{\text{BW}} := \frac{1}{2 \cdot \pi \cdot R \cdot C} \cdot 10^{\left(\frac{80 + 20 \cdot \log\left(\frac{1}{11}\right)}{20} \right)}$$

$$t_{\text{r}} := \frac{\frac{(\ln(0.9) - \ln(0.1))}{(2 \cdot \pi)}}{f_{\text{BW}}}$$
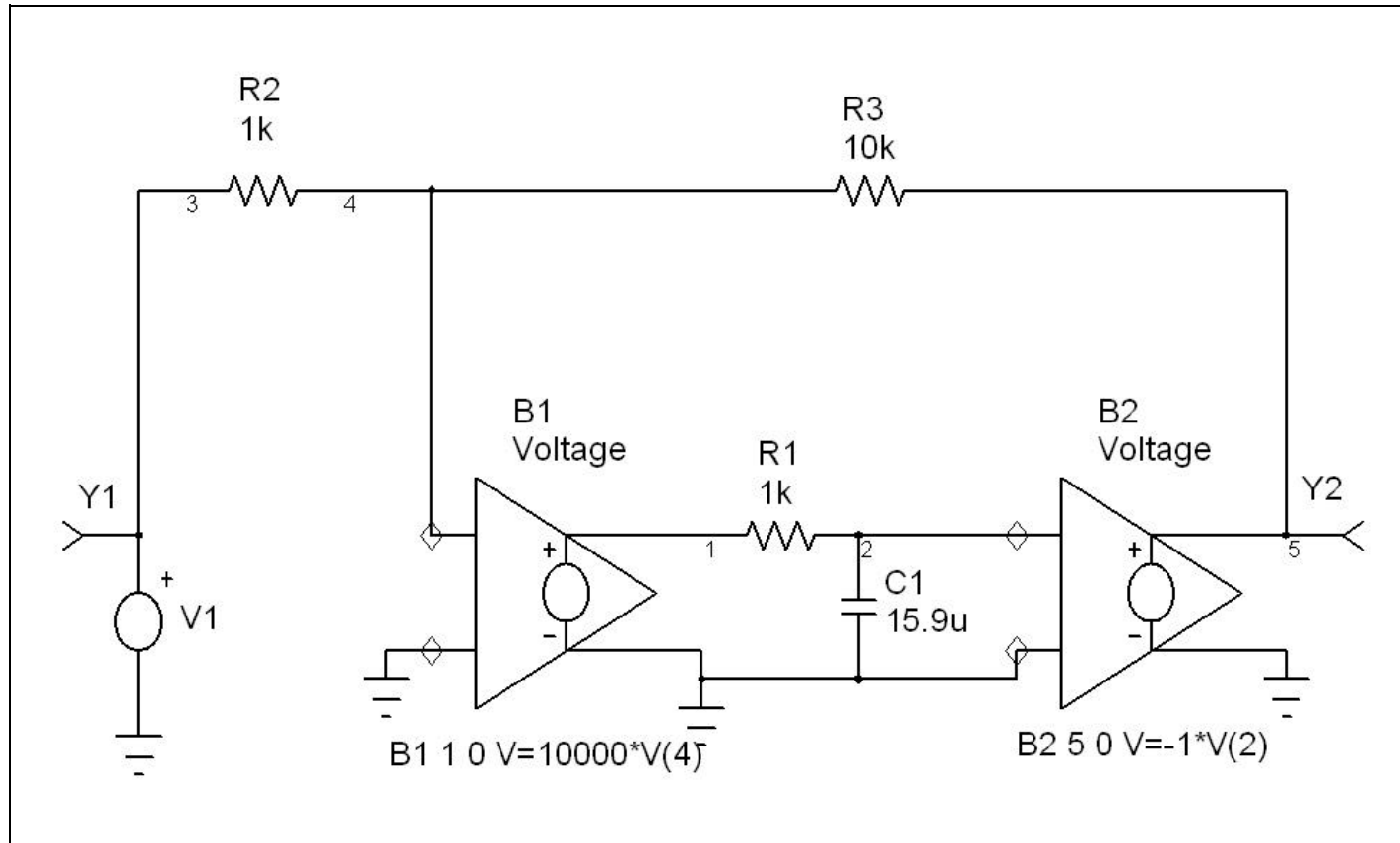
$$t_{\text{r}} = 3.842946 \times 10^{-5} \quad \text{where} \quad \frac{(\ln(0.9) - \ln(0.1))}{(2 \cdot \pi)} = 0.349699$$



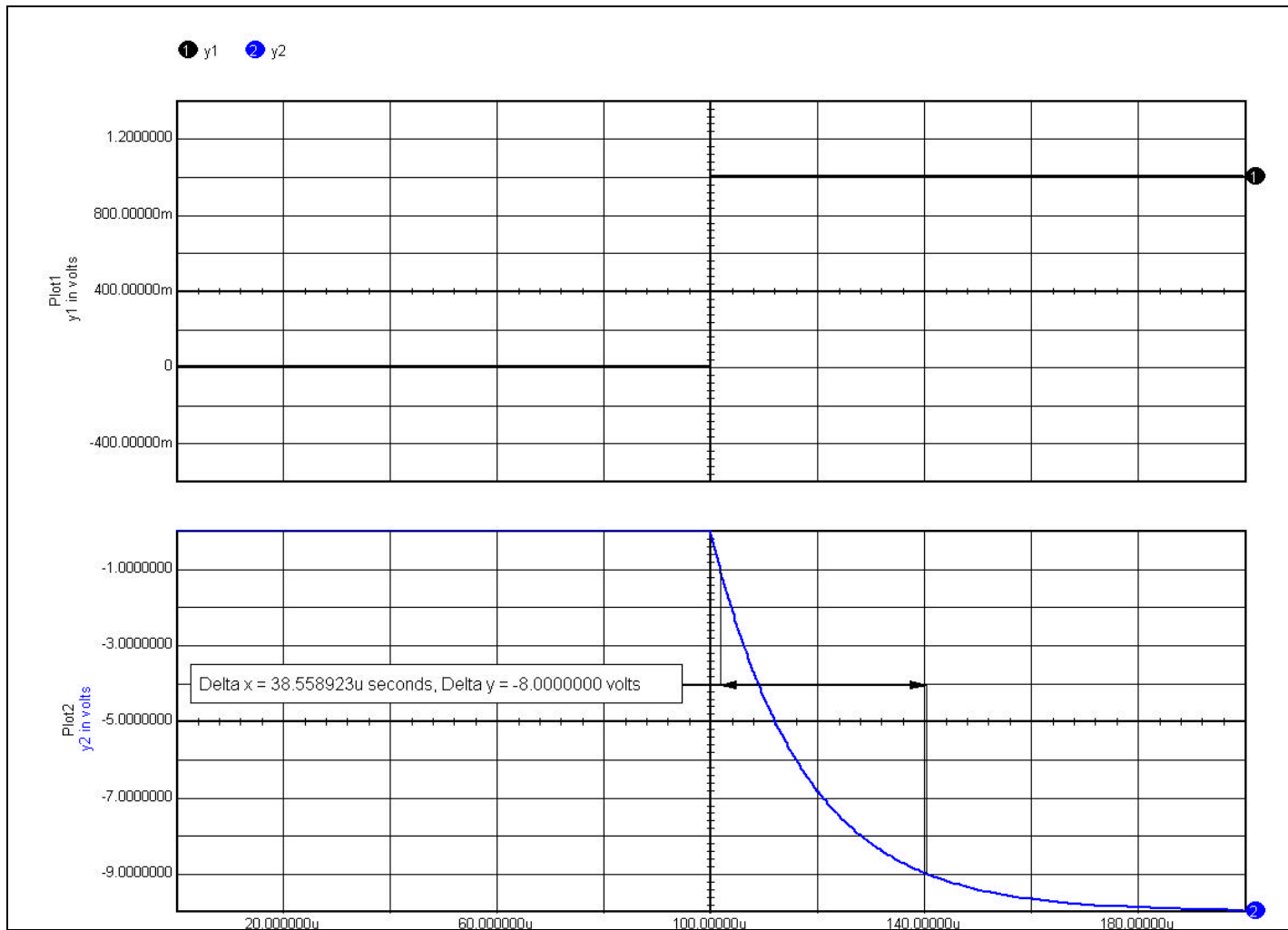Now we will simulate the above circuit and compare the rise time result with the predicted performance.



Success! Simulation matches prediction.